
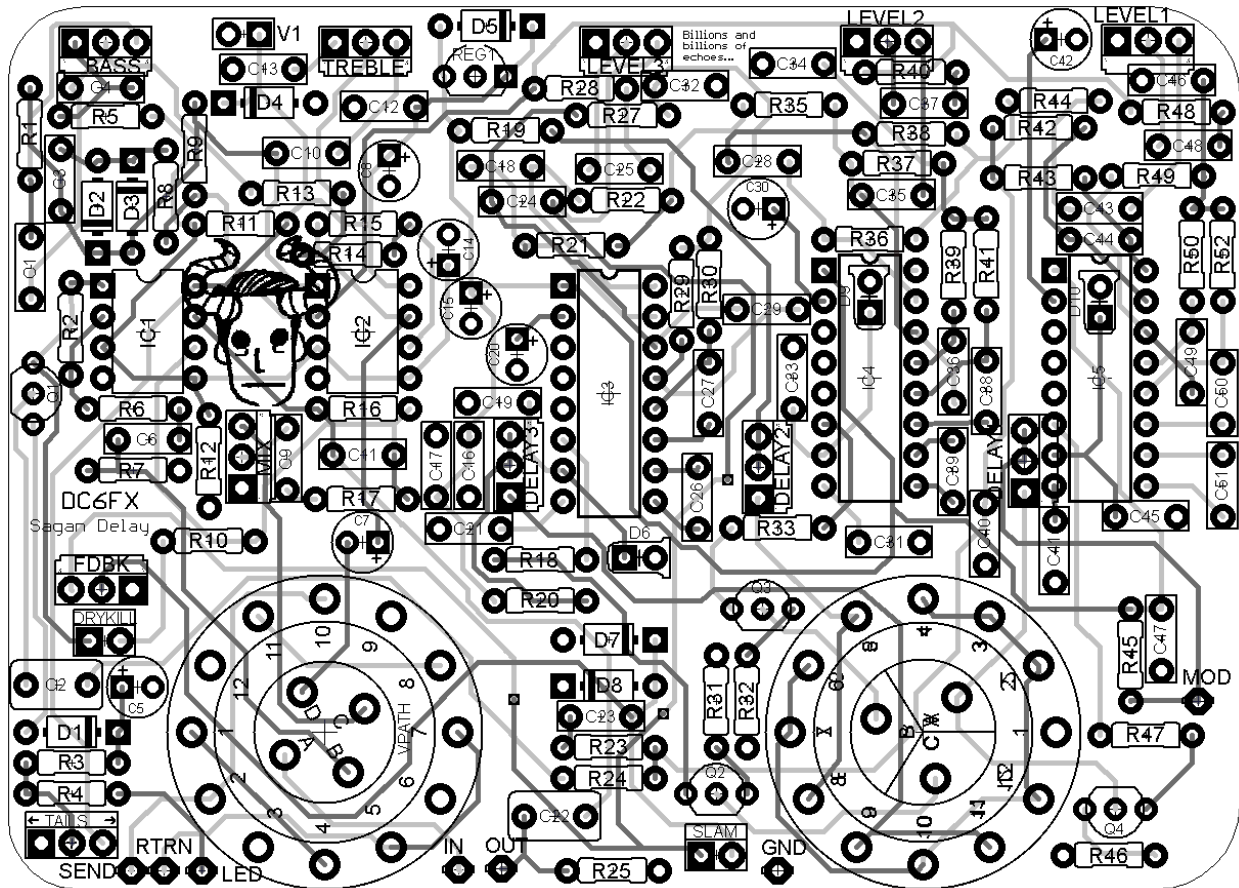


# SAGAN DELAY

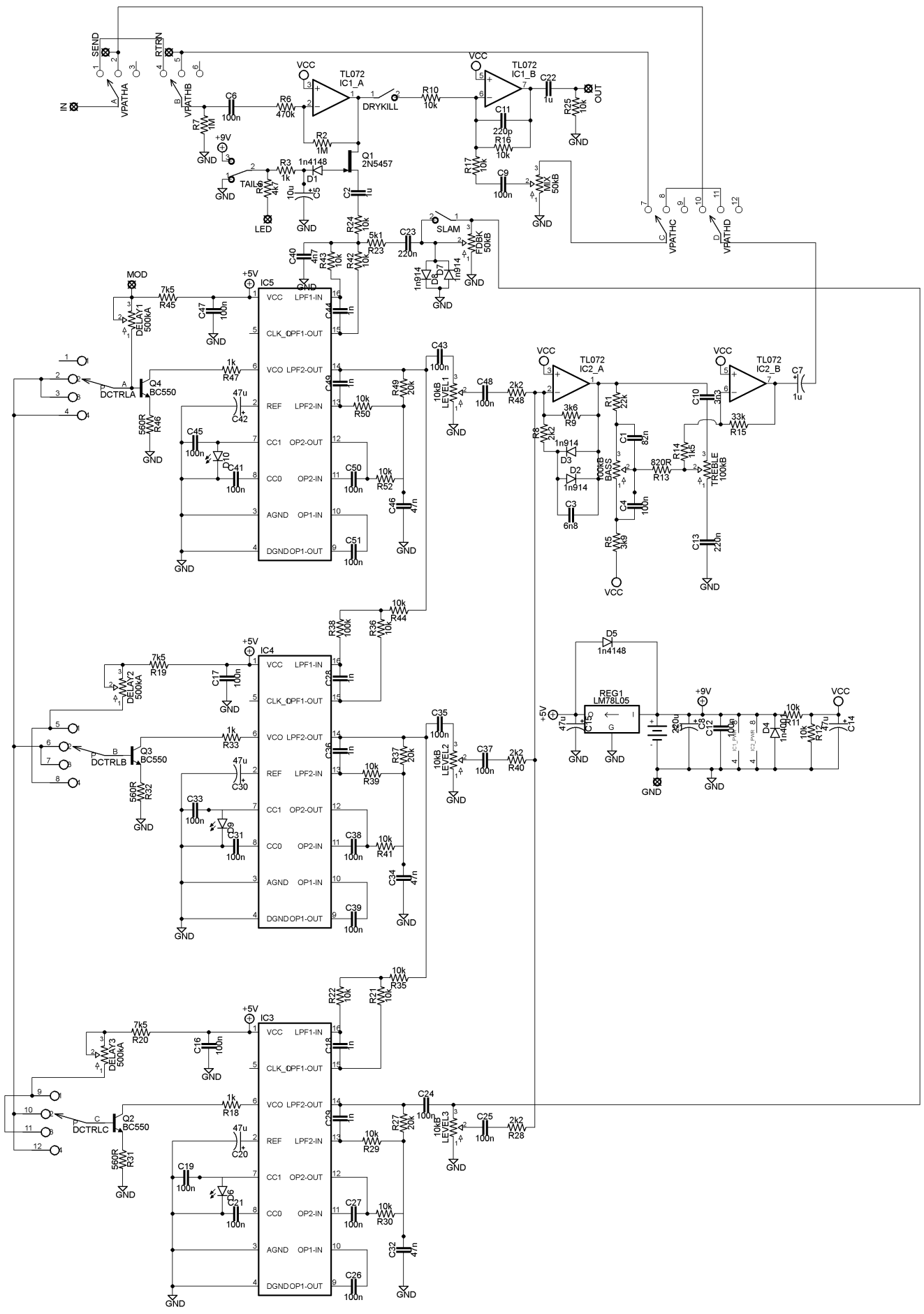

I've been jonesing for a Roland Space Echo for a long time. I'll never get one though. There's too much upkeep and the increasingly futile search for expensive replacement tape, and my wife would blow a gasket if I spent grocery money on a fancy tape player. Instead, I tried to design a circuit to emulate the heart and soul of a Space Echo. Three PT2399s emulate the three playback heads of the Space Echo, symmetrical clipping dirties up the delay a little, and there is a possibility to add reverb to the delay through send and return jacks. But why stop there? Let's make things weird. Instead of a rotary that selects what playback head is used, I added volume knobs for each PT2399 "playback head" for more nuanced level control than "on" and "off." I also allowed for each PT2399 to have an independent delay time with a turn of a rotary knob (maybe think of it as three Echoplexes in series, with different delay times?). Let's also add a SLAM! footswitch for instant feedback oscillation and the possibility to add modulation to the delay.

Delay times range from pseudo-reverb, to slapback echo, to galloping rhythms. To remind you of the digital roots of this beast, the maximum delay time introduces all the hiss and gurgling familiar with PT2399s. I figure these noises could be fun to fiddle around with. Also, the feedback oscillation gets a little grainy, but if the Boss RE-20 feedback can't nail the authentic sound, I won't have a problem if this can't either!



RESISTORS				CAPACITORS				ELECTRO CAPS			POTS	
R1	22k	R27	20k	C1	82n	C33	100n	C5	10u	BASS	100k B	
R2	1M	R28	2k2	C2	1u	C34	47n	C7	1u	DELAY1	500k A	
R3	1k	R29	10k	C3	6n8	C35	100n	C8	220u	DELAY2	500k A	
R4	4k7	R30	10k	C4	100n	C36	1n	C14	47u	DELAY3	500k A	
R5	3k9	R31	560R	C6	100n	C37	100n	C15	47u	FDBK	500k A	
R6	470k	R32	560R	C9	100n	C38	100n	C20	47u	LEVEL1	10k B	
R7	1M	R33	1k	C10	3n3	C39	100n	C30	47u	LEVEL2	10k B	
R8	2k2	R35	10k	C11	220p	C40	4n7	C42	47u	LEVEL3	10k B	
R9	3k6*	R36	10k	C12	100n	C41	100n	DIODES		MIX	50k B	
R10	10k	R37	20k	C13	220n	C43	100n	D1	1N4148	TREBLE	100k B	
R11	10k	R38	100k	C16	100n	C44	1n	D2	1N914	SWITCHES		
R12	10k	R39	10k	C17	100n	C45	100n	D3	1N914	DELAY SYNC	3P4T ROTARY	
R13	820R	R40	2k2	C18	1n	C46	47n	D4	1N4001	DRYKILL	SPDT	
R14	1k5	R41	10k	C19	100n	C47	100n	D5	1N4148	SLAM	SPST	
R15	33k**	R42	10k	C21	100n	C48	100n	D6	GREEN LED 3MM	MOMENTARY FOOTSWITCH		
R16	10k	R43	10k	C22	1u	C49	1n	D7	1N914	TAILS	DPDT	
R17	10k	R44	10k	C23	220n	C50	100n	D8	1N914	FOOTSWITCH		
R18	1k	R45	7k5	C24	100n	C51	100n	D9	GREEN LED 3MM	VPATH	4P3T ROTARY	
R19	7k5	R46	560R	C25	100n			D10	GREEN LED 3MM	REGULATOR		
R20	7k5	R47	1k	C26	100n	Q		IC		REG1	LM78L05	
R21	10k	R48	2k2	C27	100n	Q1	2N5457	IC1	TL072			
R22	10k	R49	20k	C28	1n	Q2	BC550	IC2	TL072			
R23	5k1	R50	10k	C29	1n	Q3	BC550	IC3	PT2399			
R24	10k	R52	10k	C31	100n	Q4	BC550	IC4	PT2399			
R25	10k			C32	47n			IC5	PT2399			

\* R9's value controls how much "tape saturation" distortion affects the delay signal. This value can be played with to taste. I have played with a range of 1k5-4k7 and settled on 3k6. The higher the value, the more the gain and clipping is heard.

\* \* R15's value might need adjusting to boost the volume after the tone circuit. My board has a 33k, but the value might have to change if you decide to tweak R9. If you select a lower value for R9, you will need a higher value R15 to boost the signal after the tone circuit.

D6 and D9 are actually not needed and can be omitted since D10 limits the clipping at the first delay chip. D10 should be on the pot side of the PCB.

There also doesn't seem to be any difference in sound if D7 and D8 aren't there, so they can be ignored.

I originally had the idea to use the 4P3T rotary in only two positions, but a third position could be used to bypass the reverb altogether and not have a pedal plugged in to the

send and return jacks. To get the third position, make a jumper between pads 3 and 6 and another jumper for pads 9 and 12.

### PADS

SEND= Send jack; I connected this pad to the input of a reverb pedal

RTRN= Return jack; I connected this pad to the output of a reverb pedal

IN= Connects to input jack

OUT=Connects to output jack

MOD= Connect to a modulation board of your choice. This is directly attached to the first PT2399. If all the delay chips are in sync, they will all be affected. If a PT2399 is independent of the first PT2399, its current won't be affected.


LED= connects to + leg of status LED, R4 is the current limiting resistor. The - leg of the LED can be attached to the DPDT footswitch to go to ground when activated.

GND= A courtesy ground. Can be connected to the input jack to ground all the jacks.

V1= Connects to the DC jack. The square pad connects to +9V, the round pad to ground.

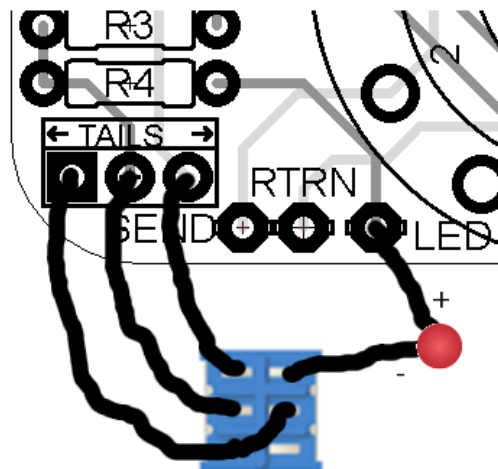
### DPDT Footswitch Connections

For the TAILS switch, connect the innermost pad to lug 1 of the DPDT, the middle pad to lug 2, and the square ground pad to lug 3. Add a jumper to connect lug 3 and lug 5. The - leg of the LED connects to lug 4.



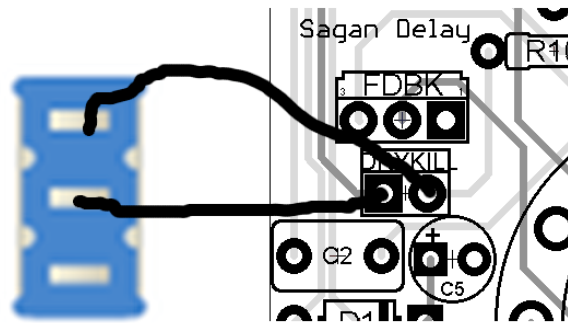
### Connecting the SPDT to the DRYKILL pads

The DRYKILL switch does exactly what it sounds like; it removes the clean signal from the output so that you only hear delay sounds. If you want to omit this switch, add a jumper between the two pads.




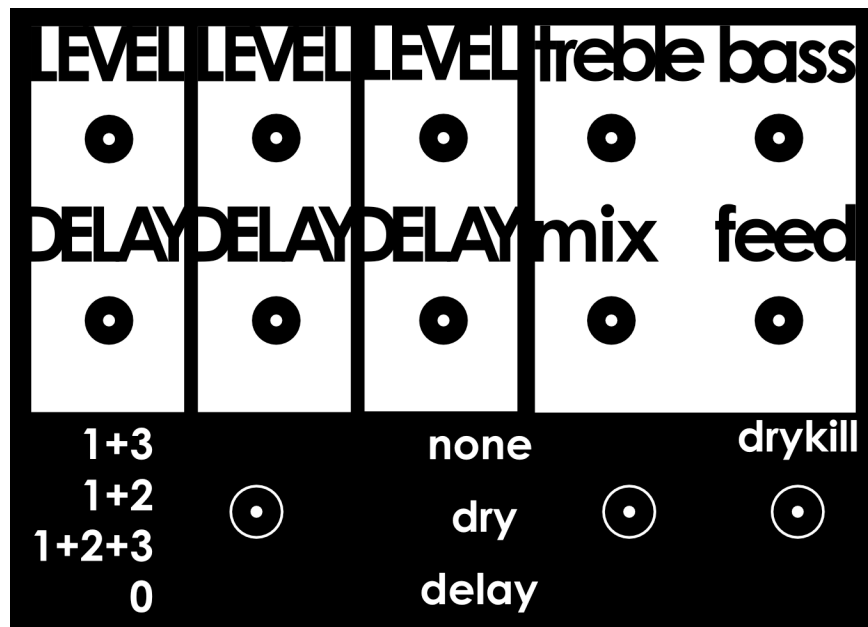Here is an idea I have for a faceplate. It can be used as a drill template. Since the pots are solder-lug, you can do whatever you want, but it does help to give you a reference for those rotary switches.


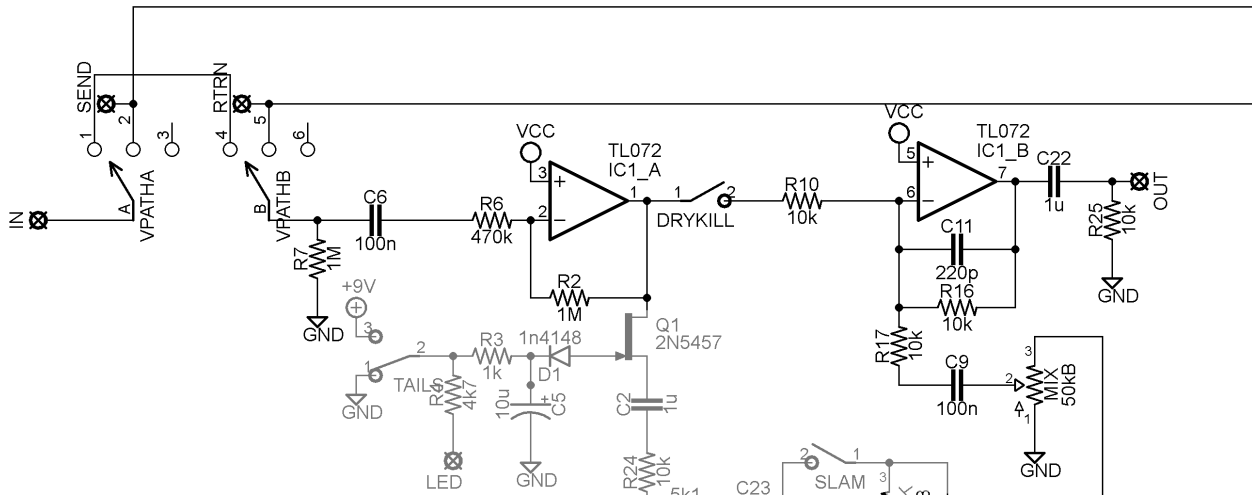
## So, how does it work?

Even though I am not an engineer and have only been dabbling in circuitry for a couple years now, I will attempt to explain what the heck is going on.




The first part of the circuit is fairly self-explanatory. The input signal goes through the SEND/RETURN rotary. Starting at the most CCW position, the signal flows as follows:

Position 1- The dry signal goes on to the op-amp unaffected, the delay signal goes through the send and return jacks before the MIX pot.

Position 2- The dry signal goes through the send and return jacks BEFORE entering the delay circuitry. If using a reverb pedal for the send/return, the reverb will be processed by the delay for some eerie atmospherics.

**SUPER SECRET** Position 3- The send and return jacks will be avoided altogether. This can only be achieved if you add a jumper from lug 3 to 6 and a jumper from lug 9 to 12 on the rotary. If you don't want this position, make sure you set the washer on the rotary to only click once.

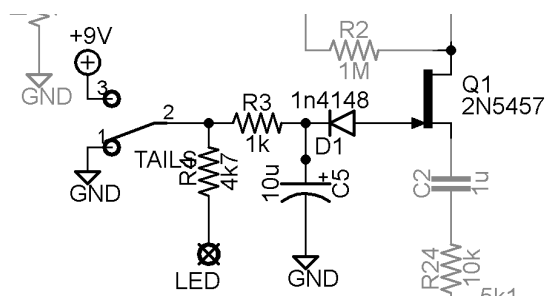After the rotary madness, the dry signal is split at pin 1 of IC1. The dry signal moves to the next part of the IC and down toward the delay circuit when activated. The wet signal joins back with the dry through the MIX pot and then to the output jack.



Following the signal down the delay path, we encounter the tails switching system.

Without getting too technical (and exposing how little knowledge I actually have on the matter), Q1 acts as a gate for the signal from the op-amp. When the footswitch is


engaged, the 9V “opens” the gate to allow the dry signal into the delay circuitry. When the gate is closed, the remaining signal processed in the delay circuit continues to work its way out the signal path with any new dry signal unaffected by the delay.


Here is where the circuit gets interesting. The PT2399 delay times are controlled through current mirroring when in sync with each other, but each successive PT2399 gets its input signal from the output of the previous PT2399, emulating the stagger of the playback heads of a Roland Space Echo. Each PT2399 output also has its own LEVEL pot. The Space Echo had a rotary to select which tape heads were used, but this design allows for more subtle delay rhythms by allowing for more volume options per delay chip than on or off.

The real fun is with the DELAY SYNC rotary. It selects what delays are synced with the first PT2399. When one or both of the subsequent PT2399s are synced to the first chip, they are controlled by the DELAY knob of the first PT2399. An unsynced PT2399 relies on its own DELAY pot. Think of it as a Space Echo where you can wiggle each tape head for funky rhythms. You can get interesting swing in the delay line.

Here are the rotary settings, starting at position 1 and moving clockwise:

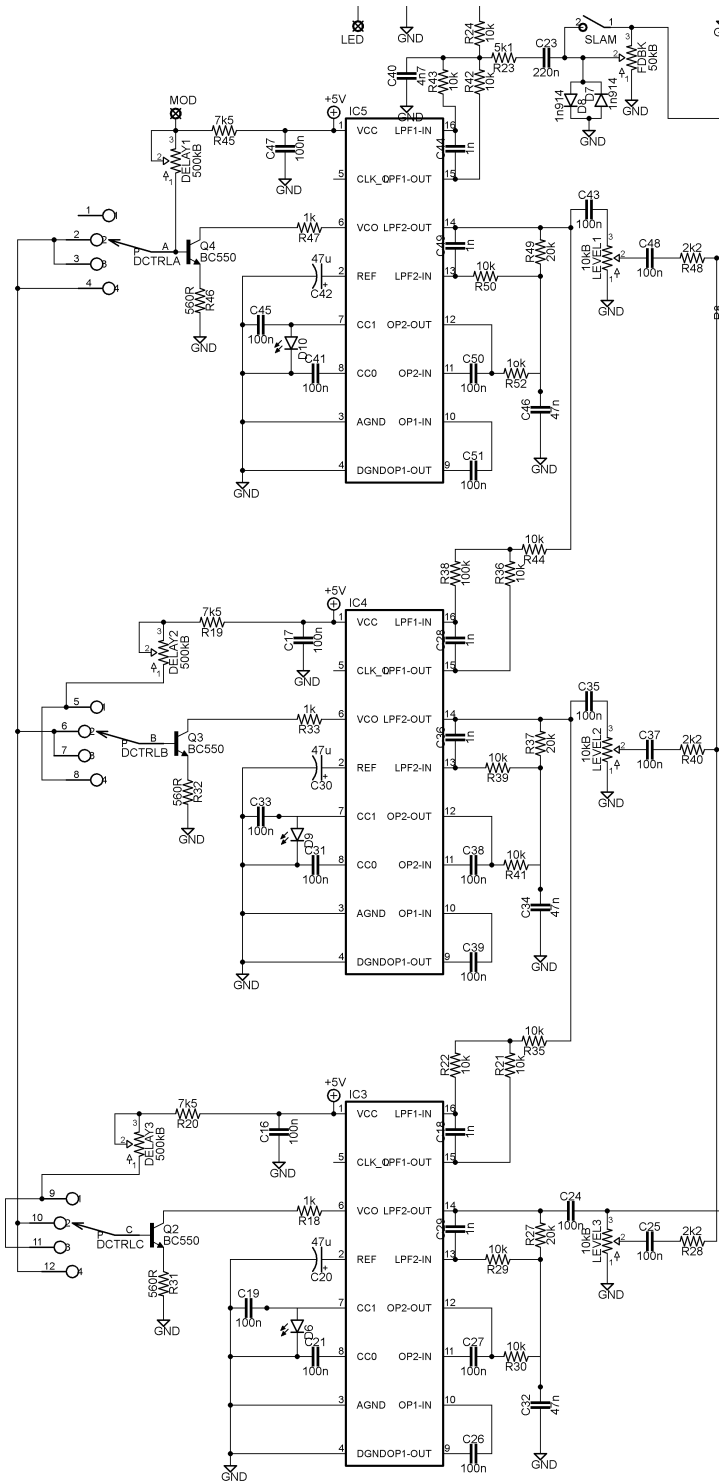- Position 1: All 3 PT2399s unsynced. Each DELAY pot works.
- Position 2: All 3 PT2399s synced. Only DELAY pot 1 is used to control delay time.
- Position 3: PT2399 1 & 2 synced, 3 is independent.
- Position 4: PT2399 1 & 3 synced, 2 is independent.



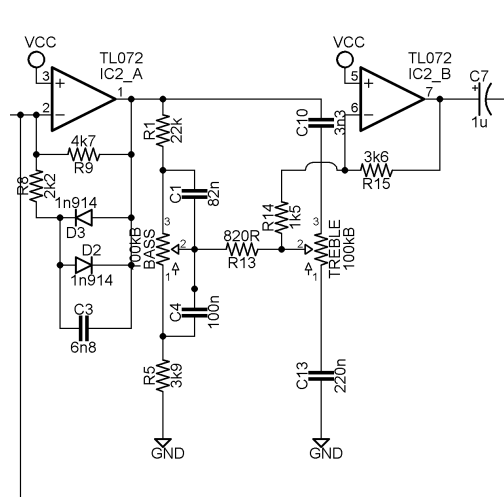

Each output of the PT2399 ends up at the saturation/EQ stage (the output of the third PT2399 also forms the feedback loop and circles back to the first PT2399). This is a modified idea from an Ibanez DE-7 (and Madbean's Zero Point Super Deluxe) with a Baxandall-style equalization. The signal goes through symmetrical clipping to make the sound a little bit grainier then goes through the EQ before regaining any lost volume through the second half of the op-amp. The values for the EQ might be a little bizarre, but it allows for a drastic reduction of highs and a slight boost in the lows of the delay signal. The harsh cut of the TREBLE pot allows for a warm, worn tape sound while taming some of the digital noise of the PT2399s at longer delay times. After leaving this stage, the signal passes through the send/return rotary and to the MIX pot.

### MISCELLANEOUS NOTES

- The transistors Q2, Q3, and Q4 need to be inserted opposite to the way the silk screen is printed (the flat side of the transistor should be on the curved side of the silk screen). I suggest you use sockets to be safe. If you insert the transistors in the way the silk screen suggests, the delay time will be extremely short.
- Due to all the pots being solder-lug (sorry!) and the tightness of the build, I would suggest soldering the wires for the DELAY pots before soldering in the capacitors.
- The slam switch is easy to install. One of the pads for the switch goes to one of the footswitch lugs, and the other pad goes to the other lug.
- While my main focus for the send and return jacks was for a reverb pedal, other pedals can theoretically be hooked up as well. I attached an Electro-Harmonix Nano Stone phaser to the send and return jacks, and it worked. Results may vary. Experiment!
- I crammed my prototype into a 1590XX enclosure; the modulation and reverb pedal are in their own enclosures. It was a tight fit with standard 1/4" jacks, but I managed to fit all 5 jacks (In, Out, Send, Return, and Modulation) in there.

### ACKNOWLEDGEMENTS

Thanks to Brian at Madbean, Josh at 1776 Effects, and Rob at Dead Astronaut FX for making their ideas available for me to pick apart and tweak. Thanks to Martin (Martan) and Cody (selfdestroyer) for "beta testing" and hammering down component values. And of course, thanks to my wife for enduring my prattling about delay circuits.