

DIY Anal og VC-LPF

ericarcher.net/devices/DIY-LPF

version 1.0


Build it yourself on perfboard. Use pad-per-hole "PC3" type

Basic voltage-controlled filter designed for 9V battery power.
5V max input level before distortion.

12dB / oct state variable LPF with LM13700-type OTA
Center frequency range 40Hz – 12kHz

MIX, **FREQ**, and **RESONANCE** controls

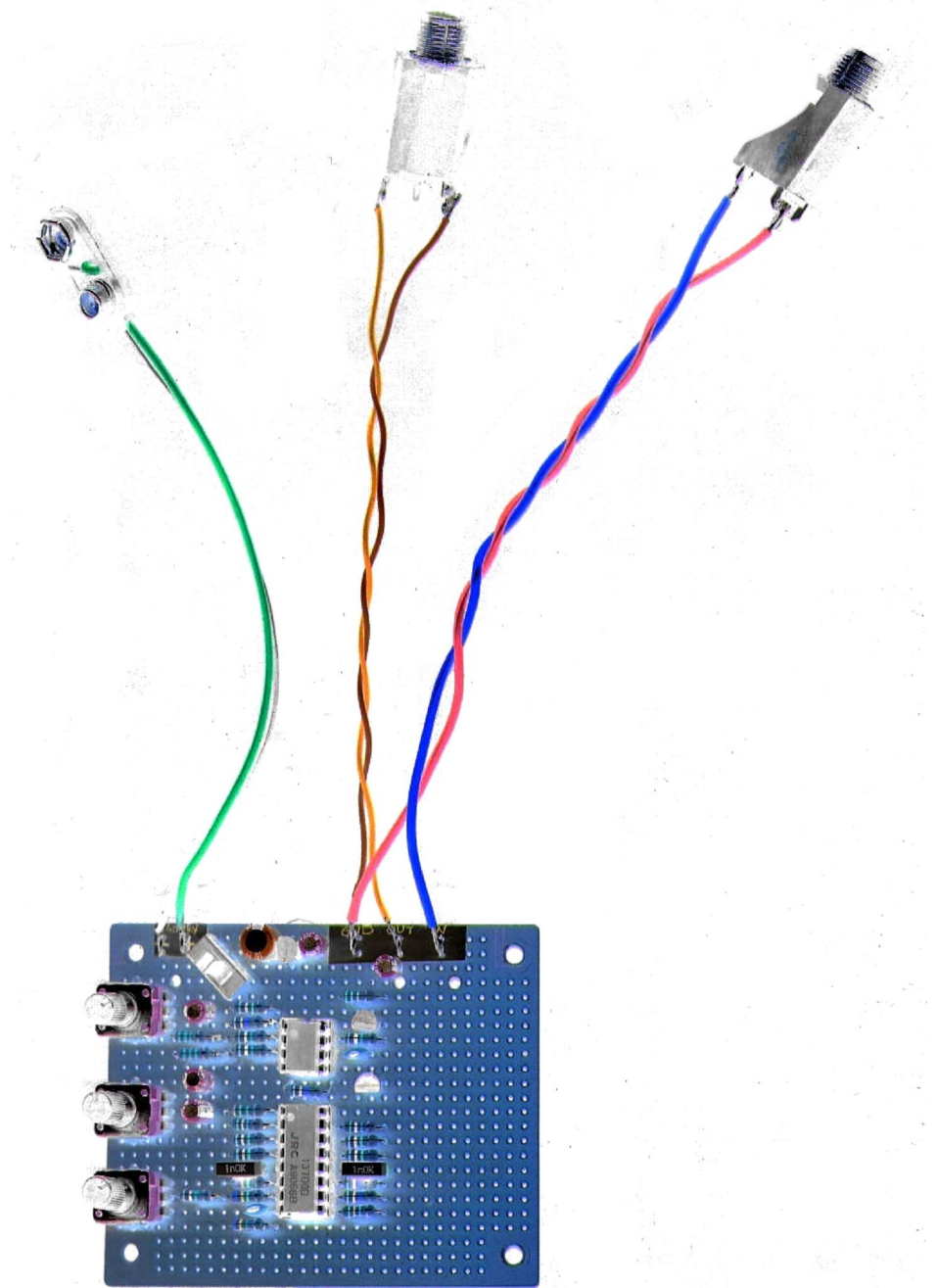Can be converted for external CV input (0..+10V)
do not use with negative voltage





9V Analog VC-LPF
DIY plans
v1.0

ericarcher.net/devices/diy-lpf

2011


	<u>qty</u>	<u>part</u>	<u>name</u>
CONNECTORS	2	1/4" jack [NYS234-3]	1/4" JACK (IN, OUT)
	1	9V snap [123-5006-GR]	
CAPACITORS	2	1n polyester 5mm LS	C1, C2
	2	22p ceramic 5mm LS	C3, C8
	5	2.2u electrolytic 4x7 mm	C4, C5, C6, C9, C10
	1	100u electrolytic 7x7mm	C7
POTENTIOMETERS	3	B10k 9mm vertical [317-2090F-10k]	FREQ, RESO, MIX
ICs	1	NJM13700D / LM13700 / LM13600 / NE5517	IC1
	1	TLE2426CLP	IC2
	1	TLC2262CP	IC3
TRANSISTORS	2	BC559B	Q1, Q2
RESISTORS	4	100k	R1, R2, R16, R21
	1	220R	R14
	4	10k	R15, R18, R20, R22
	2	33k	R17, R19
	2	5.1k	R3, R12
	3	20k	R4, R7, R10
	1	47k	R5
	5	1k	R6, R8, R11, R13, R23
	1	82k	R9
SWITCH	1	SPST slide switch (POWER) [10SP003]	SW1

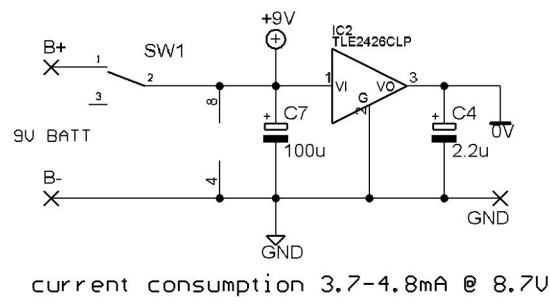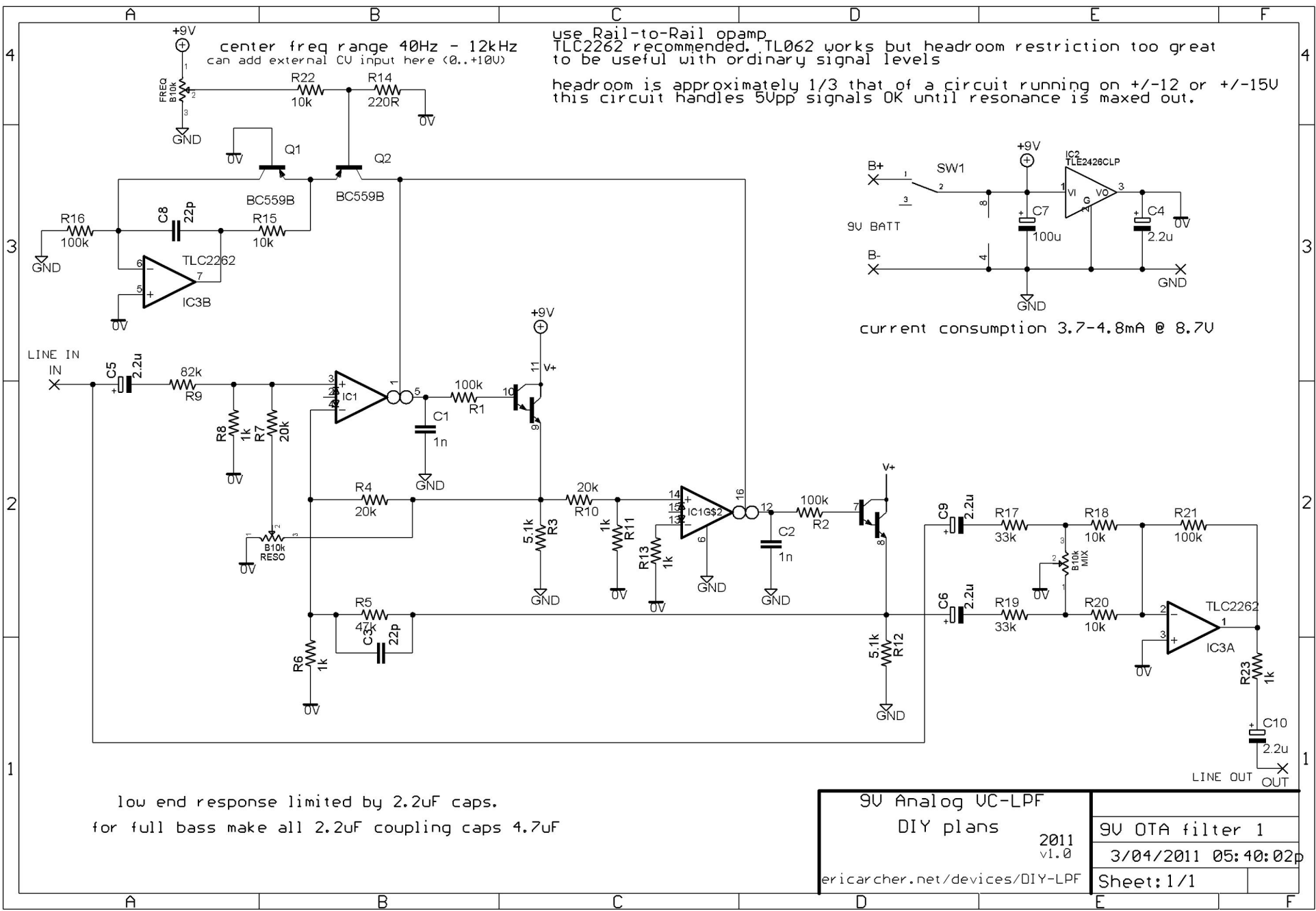use Rail-to-Rail opamp, TLC2262 recommended, TL062 works but headroom restriction too great to be useful with ordinary signal levels
 headroom is approximately 1/3 that of a circuit running on +/-12 or +/-15V
 this circuit handles 5Vpp signals OK until resonance is maxed out.




low end response limited by 2.2uF caps.
 for full bass make all 2.2uF coupling caps 4.7uF


9V Analog VC-LPF		2011 v1.0	
DIY plans		9V OTA filter 1	
ericarcher.net/devices/DIY-LPF		3/04/2011 05:40:02p	
		Sheet: 1/1	

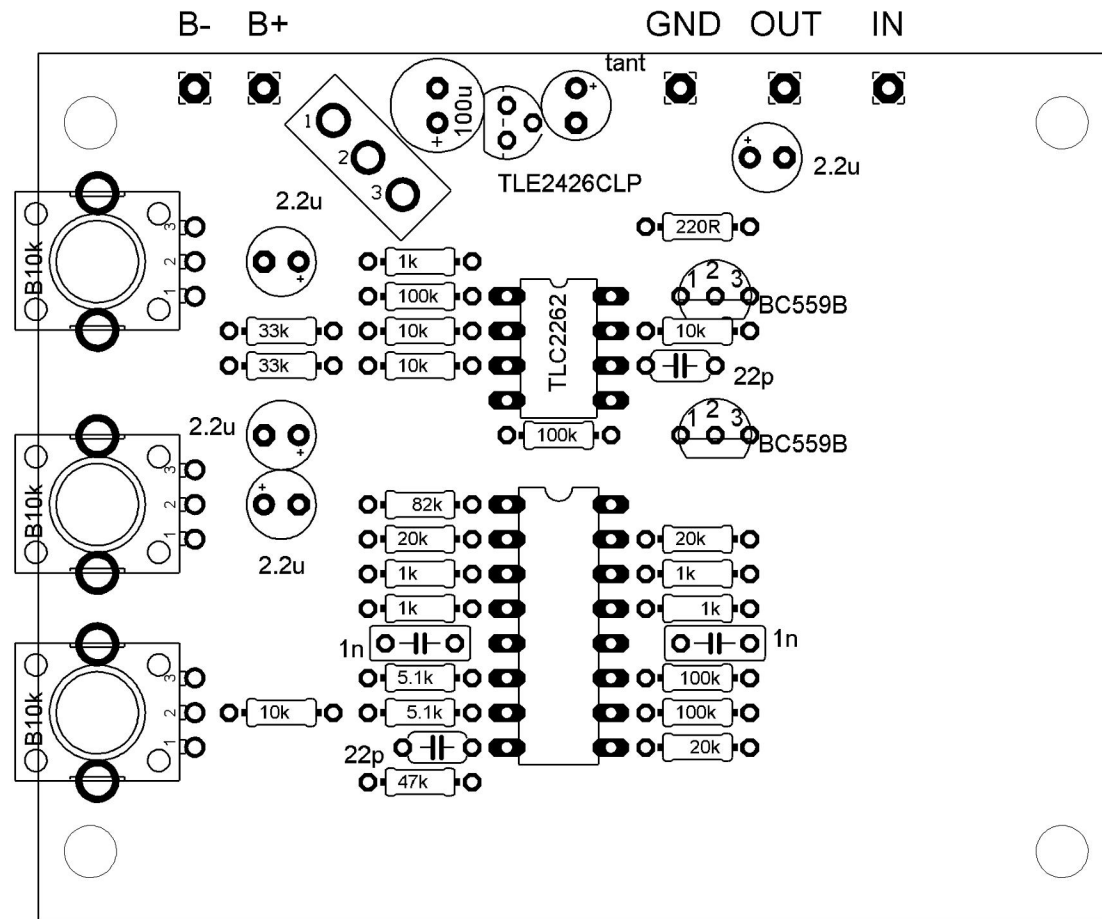


Values

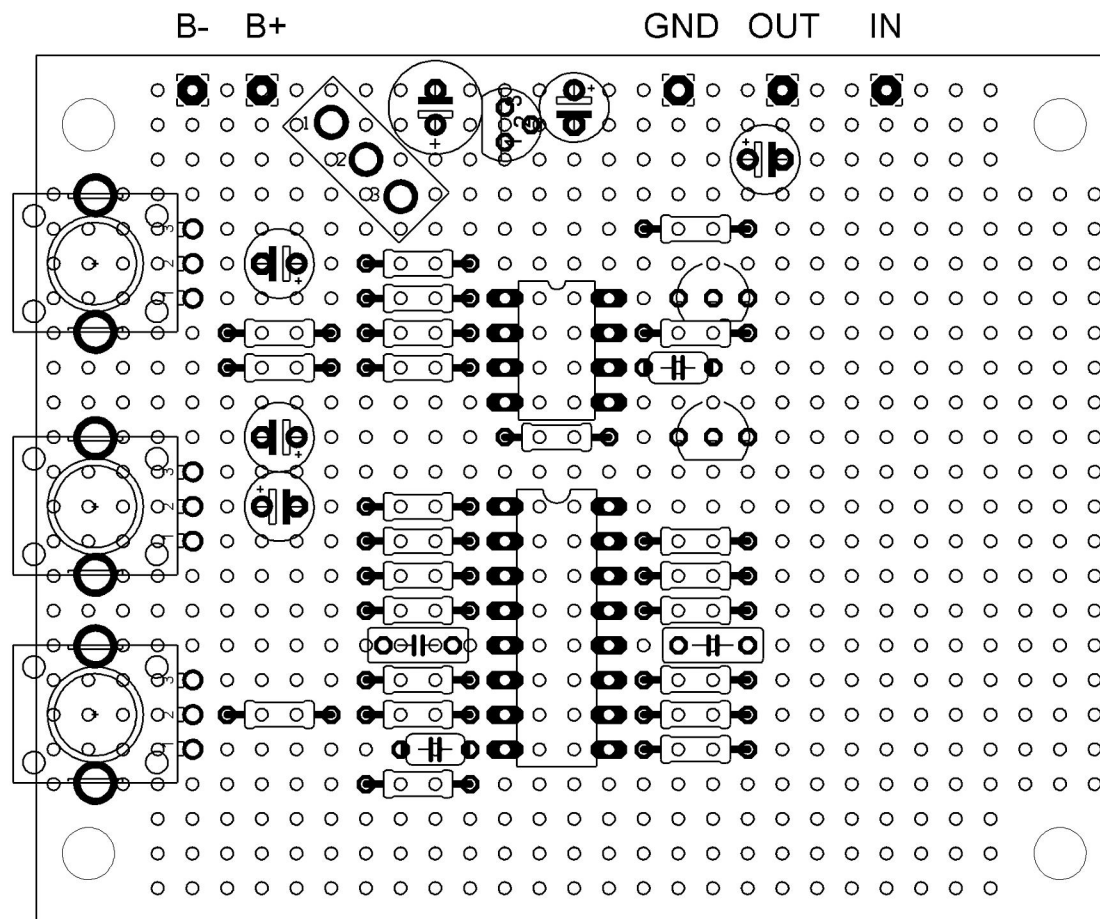


Placement

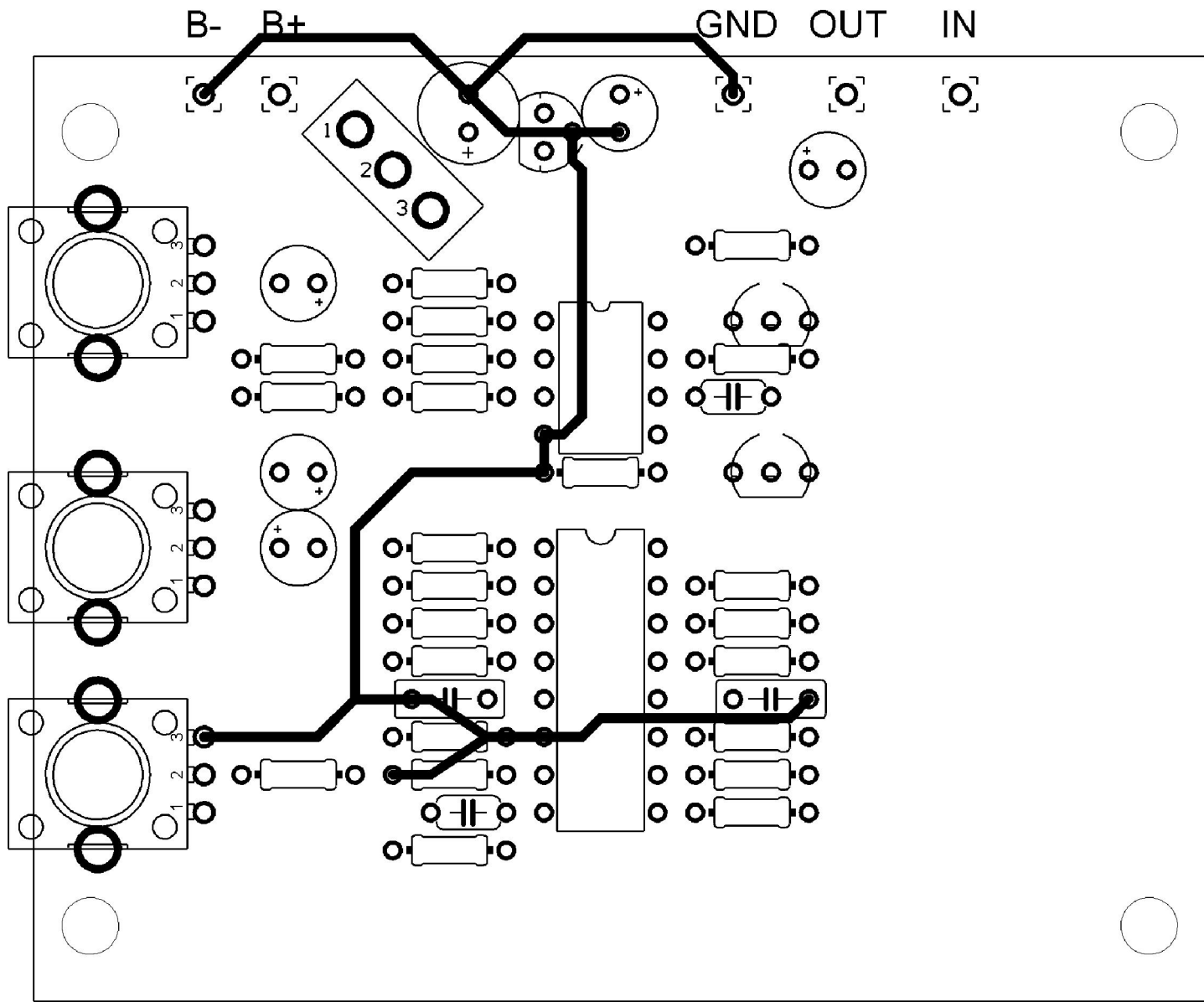


GND

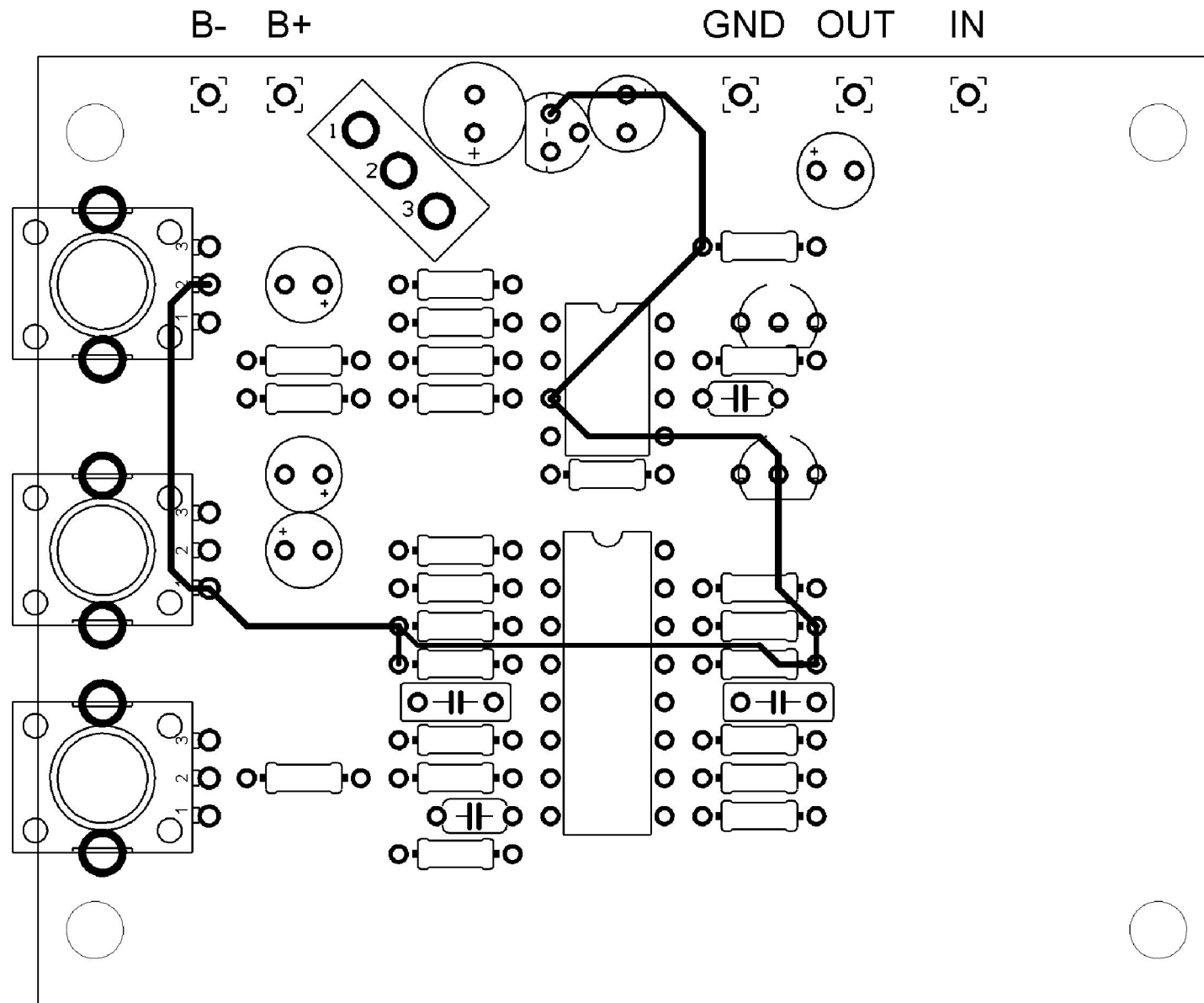


Virtual GND

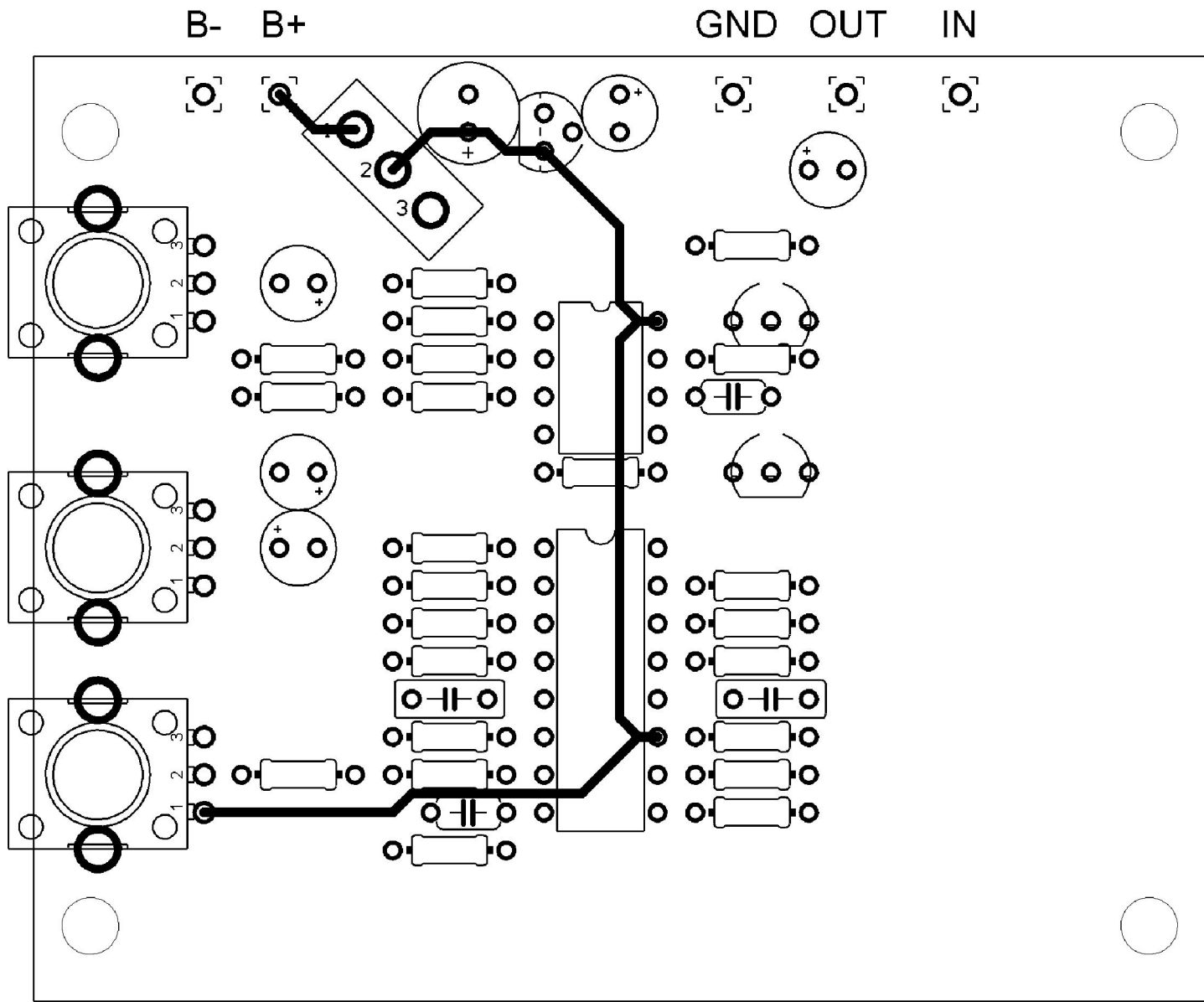


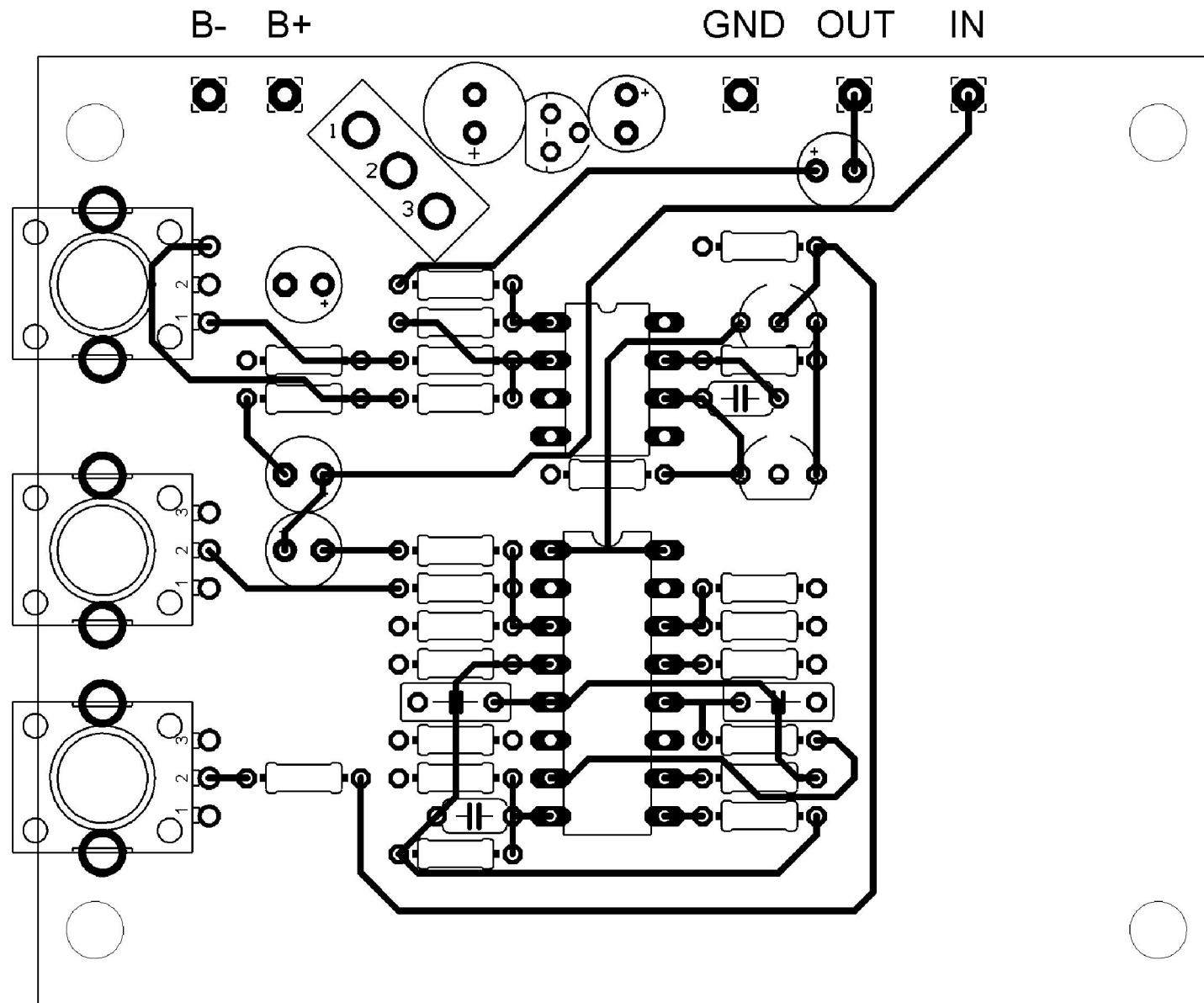


SIGNAL1

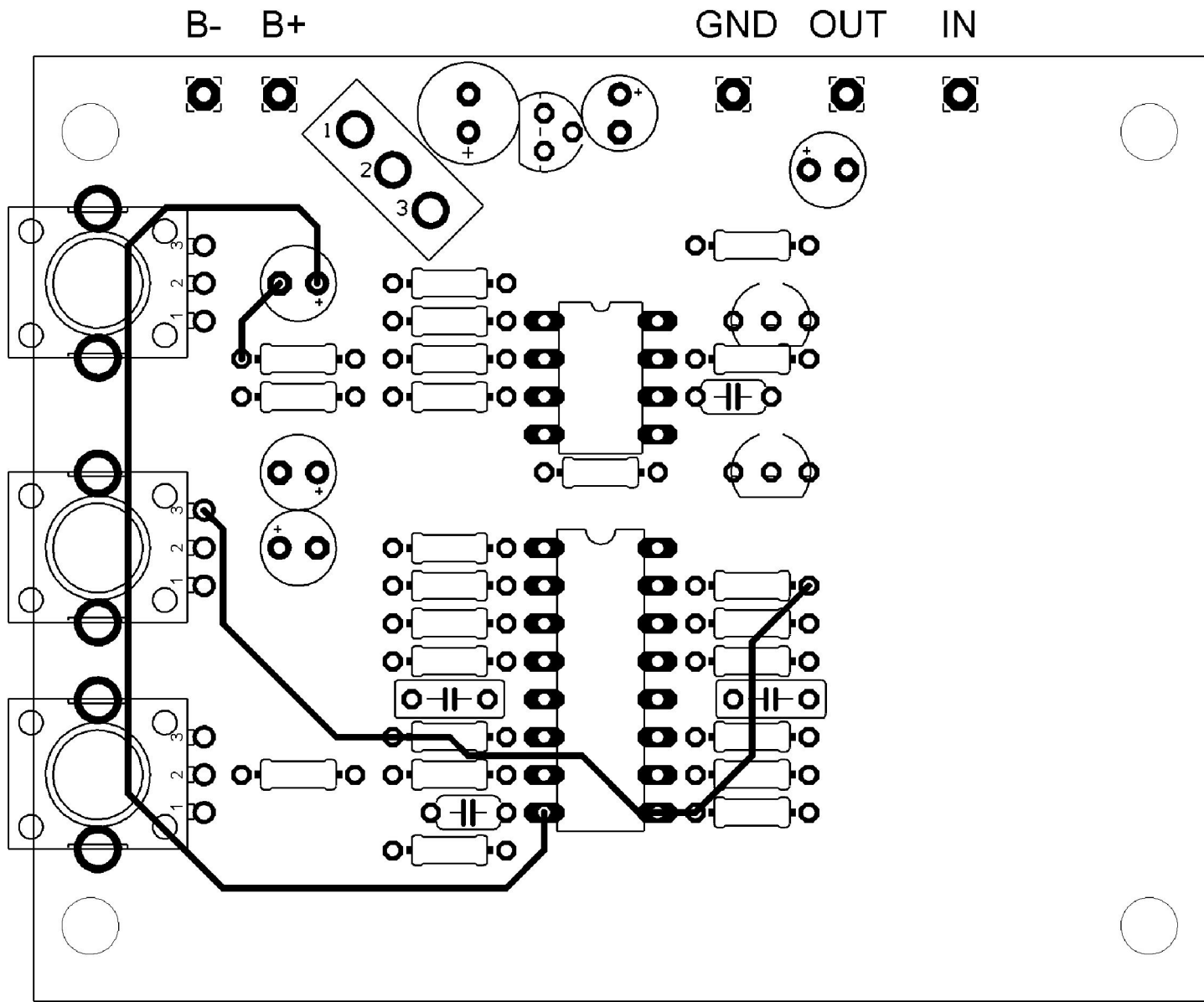

SIGNAL2

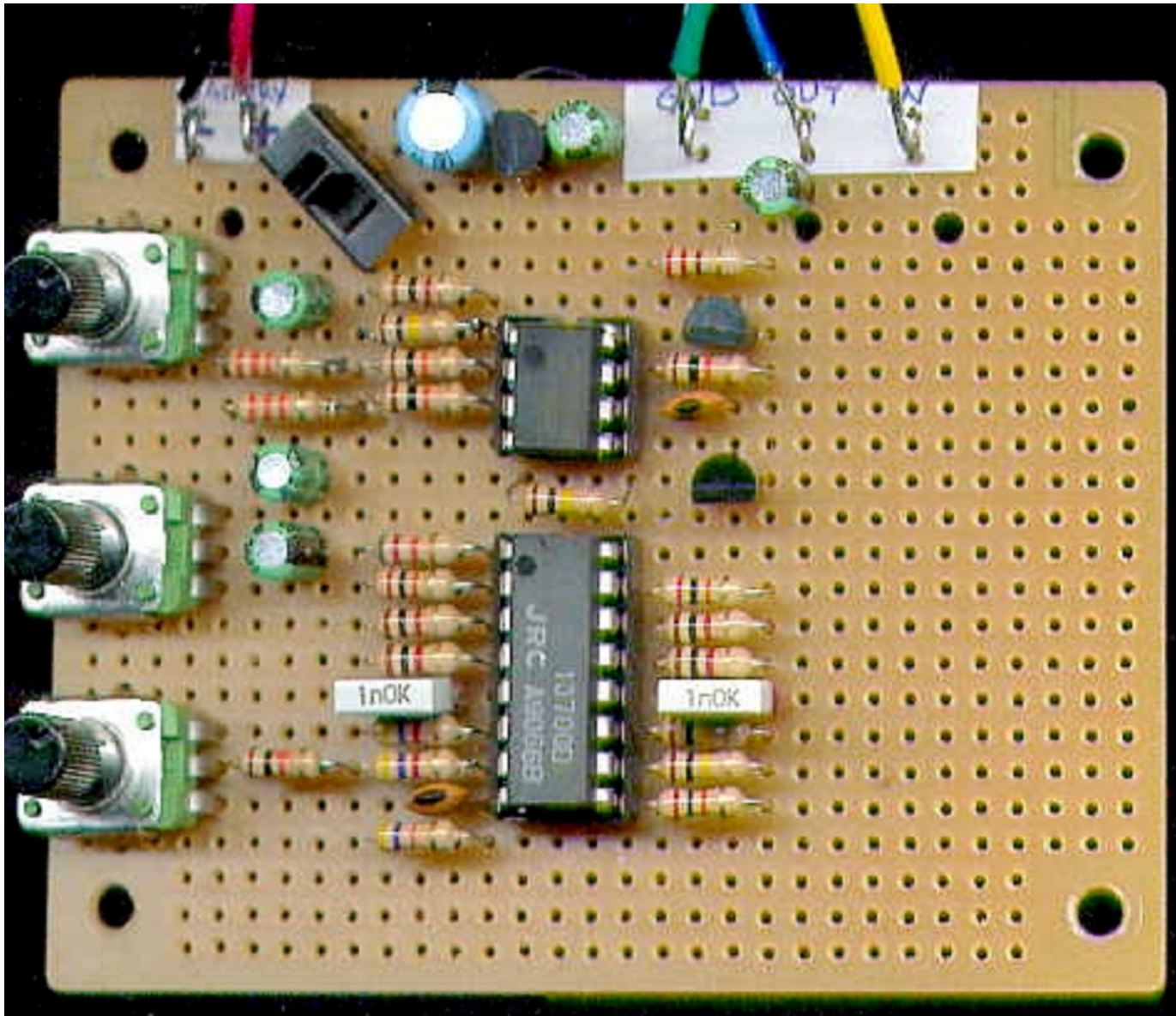

Top Side

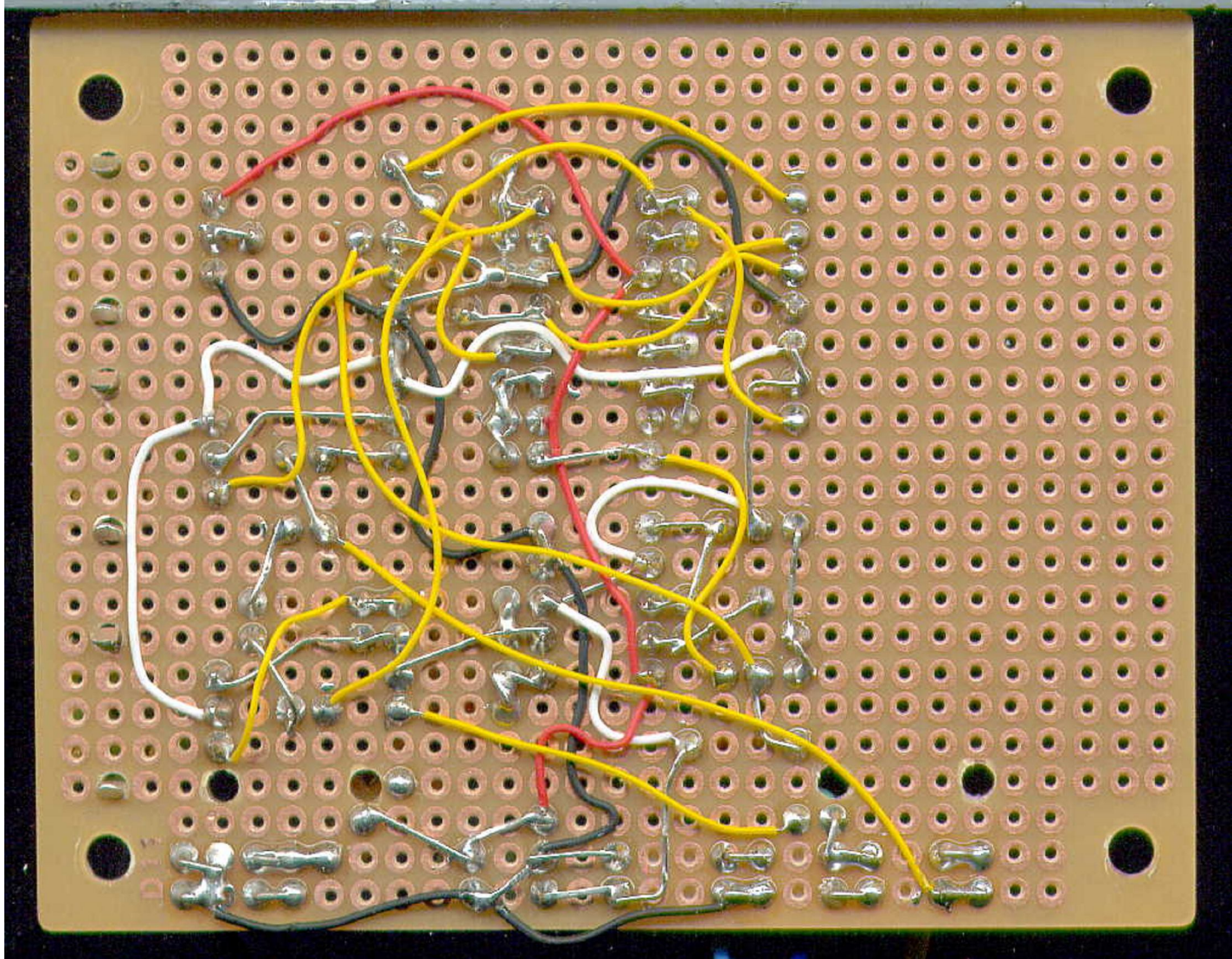

(top edge)

Bottom Side